 


FPGA & VHDL

Aula 2

VHDL: CKTs sequenciais



Flip-Flop D

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity d_ff_reset is
    Port ( clk, reset : in  STD_LOGIC;
          d : in  STD_LOGIC;
          q : out  STD_LOGIC);
end d_ff_reset;

architecture arch of d_ff_reset is
begin
    process(clk, reset)
    begin
        if(reset = '1') then
            q <= '0';
        elsif (clk' event and clk='1') then
            q <= d;
        end if;
    end process;
end arch;
```

VHDL: CKTs sequenciais

Contador binário

```
library ieee;
use ieee.std_logic_1164.ALL;
use ieee.numeric_std.ALL;

entity counter is
  generic(N: integer := 8);
  Port (
    clk,reset : in  std_logic;
    max_tick : out std_logic;
    q : out  std_logic_vector (N-1 downto 0)
  );
end counter;

architecture arch of counter is
  signal r_reg: unsigned (N-1 downto 0);
  signal r_next: unsigned (N-1 downto 0);
begin
  process(clk,reset)
  begin
    if(reset='1') then
      r_reg <= (others => '0');
    elsif (clk' event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  r_next <= r_reg + 1;
  q <= std_logic_vector(r_reg);
  max_tick <= '1' when r_reg=(2**N-1) else '0';
end arch;
```

Testbench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

entity counter_tb is
end counter_tb;

architecture arch of counter_tb is
  -- constant
  constant N: integer :=4;
  constant T: time := 20 ns;
  --Inputs
  signal clk,reset,max_tick : std_logic;
  signal q : std_logic_vector(N-1 downto 0);

begin

  -- Instantiate the Unit Under Test (UUT)
  uut: entity work.counter(arch)
    generic map(N=>N)
    port map( clk => clk, reset => reset,
      max_tick => max_tick, q => q);

  -- Clock process definitions
  clk_process :process
  begin
    clk <= '0';
    wait for T/2;
    clk <= '1';
    wait for T/2;
  end process;
  reset <='1', '0' after T/4;
end arch;
```

VHDL: CKTs sequenciais

Contador binário up/down

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter_up_down is
    generic(N: integer:=8);
    port(
        clk, reset, up: in std_logic;
        max_tick: out std_logic;
        q: out std_logic_vector(N-1 downto 0)
    );
end counter_up_down;

architecture arch of counter_up_down is
    signal r_reg : unsigned (N-1 downto 0);
begin
    process(clk, reset)
    begin
        if(reset='1') then
            r_reg <= (others=>'0');
        elsif (clk' event and clk='1') then
            if(up='1') then
                r_reg <= r_reg +1;
            else
                r_reg <= r_reg-1;
            end if;
        end if;
    end process;
    q <= std_logic_vector(r_reg);
    max_tick <= '1' when r_reg=(2**N-1) else '0';
end arch;
```

Testbench

```
library ieee;
use ieee.std_logic_1164.ALL;

--USE ieee.numeric_std.ALL;


entity counter_up_down_tb is
end counter_up_down_tb;

architecture arch of counter_up_down_tb is
    -- constants
    constant N: integer :=4;
    constant T: time := 20 ns;
    -- inputs
    signal clk,reset,up,max_tick: std_logic;
    signal q : std_logic_vector(N-1 downto 0);
begin
    -- Instantiate the Unit Under Test (UUT)
    uut: entity work.counter_up_down(arch)
        generic map( N=> N)
        port map( clk => clk, reset => reset, up => up,
            max_tick => max_tick, q => q );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
        wait for T/2;
        clk <= '1';
        wait for T/2;
    end process;

    reset <= '1', '0' after T/4;
    up <= '1', '0' after T*(2**N);
end arch;
```

Display Spartan3E

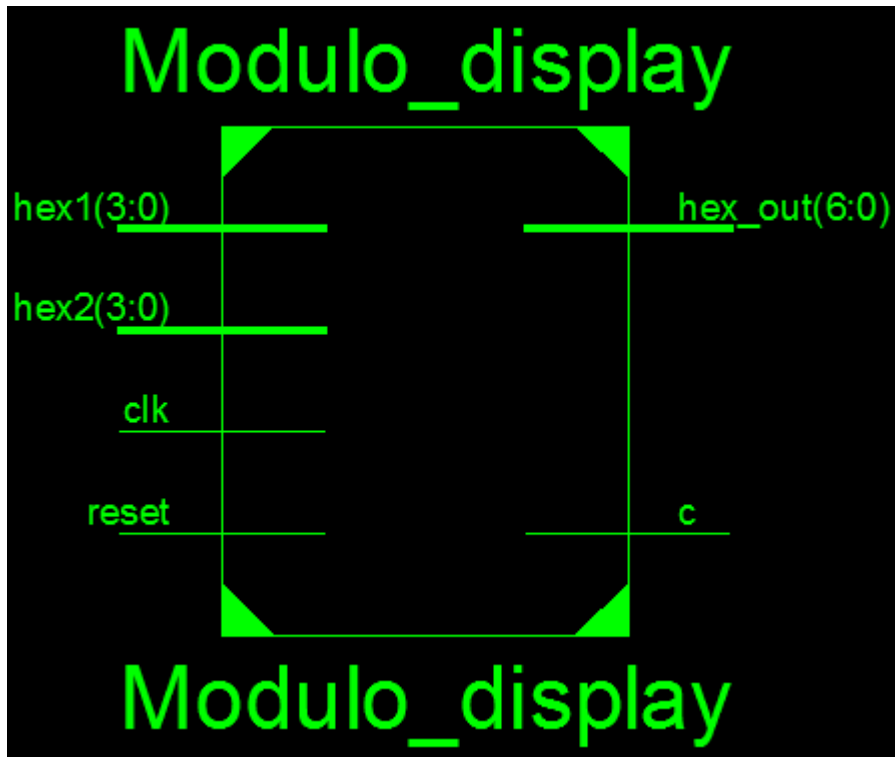

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Modulo_display is
    Port ( clk : in  STD_LOGIC;
          reset : in  STD_LOGIC;
          hex1 : in  STD_LOGIC_VECTOR (3 downto 0);
          hex2 : in  STD_LOGIC_VECTOR (3 downto 0);
          hex_out : out  STD_LOGIC_VECTOR (6 downto 0);
          c : out  STD_LOGIC);
end Modulo_display;

architecture arch of Modulo_display is
    signal clk_aux: std_logic :='0';
    signal tick: std_logic :='0';
begin
    counter: entity work.mod_m_counter(arch)
        GENERIC MAP (
            N =>19,M =>500000)
        PORT MAP(
            clk => clk,
            reset => reset,
            max_tick => tick
        );

    dis : entity work.display_7_seg(arch)
        PORT MAP(
            clk => clk_aux,
            c => c,
            hex1 => hex1,
            hex2 => hex2,
            hex7seg => hex_out
        );
end process (tick)
begin
    if (tick'event and tick='1') then
        clk_aux <= not clk_aux;
    end if;
end process;
end arch;
```

VHDL: CKTs sequenciais

Contador módulo-m

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mod_m_counter is
  generic (
    N: integer := 4; -- no. of bits
    M: integer := 10 -- mod_M
  );
  port (
    clk, reset: in std_logic;
    max_tick: out std_logic;
    q: out std_logic_vector(N-1 downto 0)
  );
end mod_m_counter;

architecture arch of mod_m_counter is
  signal r_reg: unsigned(N-1 downto 0);
  signal r_next: unsigned(N-1 downto 0);
begin
  process(clk, reset)
  begin
    if(reset='1') then
      r_reg <= (others => '0');
    elsif (clk' event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  r_next <= (others=>'0') when r_reg=M-1 else r_reg +1;
  q <= std_logic_vector(r_reg);
  max_tick <= '1' when r_reg=M-1 else '0';
end arch;
```

Testbench

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mod_m_counter_tb is
end mod_m_counter_tb;

architecture arch of mod_m_counter_tb is
  -- constant
  constant N: integer := 6;
  constant M: integer := 4;
  constant T: time := 20 ns;
  signal clk, reset, max_tick: std_logic;
  signal q: std_logic_vector(N-1 downto 0);
begin
  -- Instantiate the Unit Under Test (UUT)
  uut: entity work.mod_m_counter(arch)
  generic map (N => N, M => M)
  port map( clk => clk, reset => reset,
  max_tick => max_tick, q => q );

  process
  begin
    clk <= '0';
    wait for T/2;
    clk <= '1';
    wait for T/2;
  end process;
  reset <= '1', '0' after T/2;
end arch;
```

Timer

- *Clock* da placa:

$$f = 50 \text{ MHz}$$
$$T = 20 \times 10^{-9} \text{ s}$$


- Para : $t = 1 \text{ s}$

$$t = M \times T$$
$$M = 50000000$$

Cálculo de N:

$$2^N > M$$
$$N > 25.57$$
$$N = 26$$

Módulo Display 7 segmentos

 


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity display_7_seg is
    Port ( clk : in  STD_LOGIC;
          c : out  STD_LOGIC;
          hex1 : in  STD_LOGIC_VECTOR (3 downto 0);
          hex2 : in  STD_LOGIC_VECTOR (3 downto 0);
          hex7seg : out  STD_LOGIC_VECTOR (6 downto 0));
end display_7_seg;

architecture arch of display_7_seg is
    CONSTANT ds0 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "0111111";
    CONSTANT ds1 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "0000110";
    CONSTANT ds2 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1011011";
    CONSTANT ds3 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1001111";
    CONSTANT ds4 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1100110";
    CONSTANT ds5 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1101101";
    CONSTANT ds6 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1111101";
    CONSTANT ds7 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "0000111";
    CONSTANT ds8 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1111111";
    CONSTANT ds9 : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1100111";
    CONSTANT dsA : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1110111";
    CONSTANT dsB : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1111100";
    CONSTANT dsC : STD_LOGIC_VECTOR (6 DOWNTO 0) := "0111001";
    CONSTANT dsD : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1011110";
    CONSTANT dsE : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1111001";
    CONSTANT dsF : STD_LOGIC_VECTOR (6 DOWNTO 0) := "1110001";
    CONSTANT dsn : STD_LOGIC_VECTOR (6 DOWNTO 0) := "0000000";
    SIGNAL seg_h : STD_LOGIC_VECTOR(6 DOWNTO 0) := (others=>'0');
    SIGNAL seg_l : STD_LOGIC_VECTOR(6 DOWNTO 0) := (others=>'0');
    SIGNAL hex1Int : INTEGER RANGE 15 DOWNTO 0;
    SIGNAL hex2Int : INTEGER RANGE 15 DOWNTO 0;
begin
```


Módulo Display 7 segmentos

```
table_f: BLOCK
  BEGIN
    hex7seg    <= seg_h WHEN clk = '1' ELSE
                seg_l WHEN clk = '0';
    c <= clk;
  END BLOCK table_f;
table_h: BLOCK
  BEGIN
    hex1Int <= to_integer(unsigned(hex1));
    seg_h <= ds0 WHEN hex1Int = 0 ELSE
    ds1 WHEN hex1Int = 1 ELSE
    ds2 WHEN hex1Int = 2 ELSE
    ds3 WHEN hex1Int = 3 ELSE
    ds4 WHEN hex1Int = 4 ELSE
    ds5 WHEN hex1Int = 5 ELSE
    ds6 WHEN hex1Int = 6 ELSE
    ds7 WHEN hex1Int = 7 ELSE
    ds8 WHEN hex1Int = 8 ELSE
    ds9 WHEN hex1Int = 9 ELSE
    dsA WHEN hex1Int = 10 ELSE
    dsB WHEN hex1Int = 11 ELSE
    dsC WHEN hex1Int = 12 ELSE
    dsD WHEN hex1Int = 13 ELSE
    dsE WHEN hex1Int = 14 ELSE
    dsF WHEN hex1Int = 15 and hex1 = "1111" ELSE
    dsn;
  END BLOCK table_h;
```



```
table_1: BLOCK
  BEGIN
    hex2Int <= to_integer(unsigned(hex2));
    seg_l <= ds0 WHEN hex2Int = 0 ELSE
    ds1 WHEN hex2Int = 1 ELSE
    ds2 WHEN hex2Int = 2 ELSE
    ds3 WHEN hex2Int = 3 ELSE
    ds4 WHEN hex2Int = 4 ELSE
    ds5 WHEN hex2Int = 5 ELSE
    ds6 WHEN hex2Int = 6 ELSE
    ds7 WHEN hex2Int = 7 ELSE
    ds8 WHEN hex2Int = 8 ELSE
    ds9 WHEN hex2Int = 9 ELSE
    dsA WHEN hex2Int = 10 ELSE
    dsB WHEN hex2Int = 11 ELSE
    dsC WHEN hex2Int = 12 ELSE
    dsD WHEN hex2Int = 13 ELSE
    dsE WHEN hex2Int = 14 ELSE
    dsF WHEN hex2Int = 15 and hex2 = "1111" ELSE
    dsn;
  END BLOCK table_1;
end arch;
```