

Máquinas de estado Finitos


Computação Digital

Máquinas de Estados

- Estados
 - Situação particular na qual encontra-se uma Máquina de Estado.
 - Pode trocar de estado em função das entradas e do estado atual.
 - Cada saída apresenta um proposito independente.
- Tipos Máquina de Estados
 - Máquina de estado de Mealy.
 - Máquina de estado de Moore.


Máquinas de Estados

Máquina de estado de Mealy.

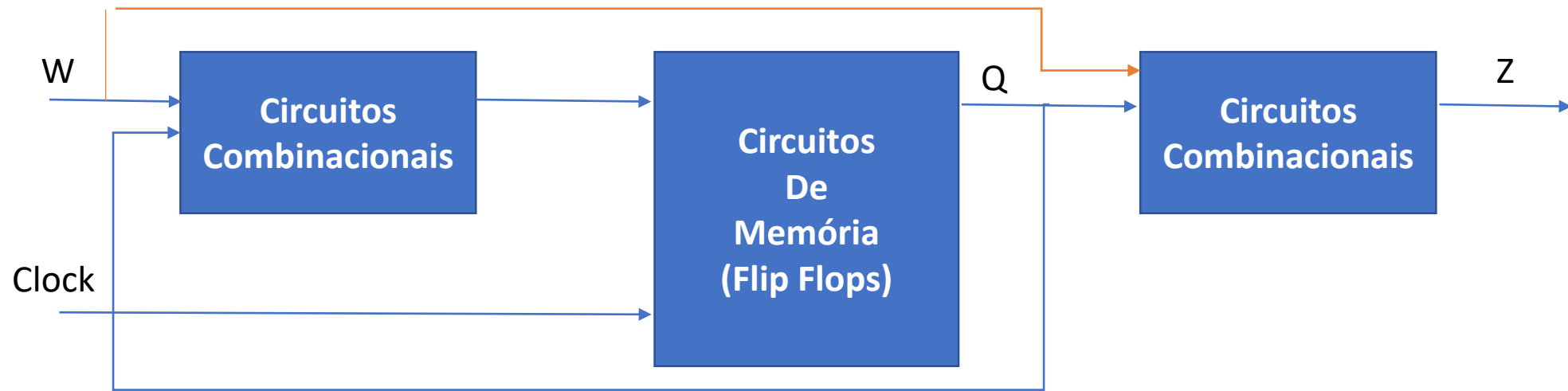

Máquinas de Estados

Maquina de estado de Moore.

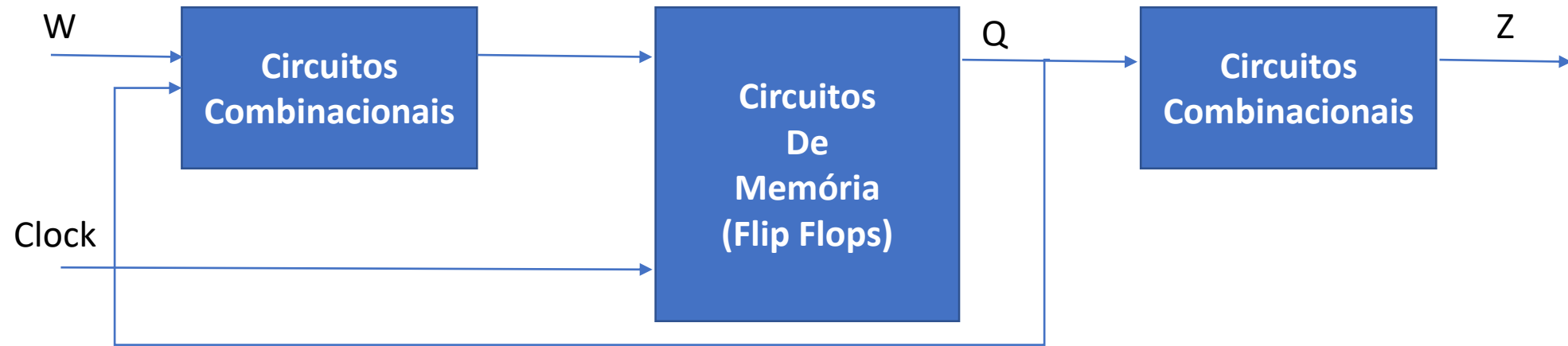


Máquinas de Estados

Diagrama de uma máquina de estado.

- Entrada : W
- Saída : Z

clock	t0	t1	t2	t3	t4	t5	t6	t7	t8	t9	t10
W	0	1	0	1	1	0	1	1	1	0	1
Z	0	0	0	0	0	1	0	0	1	1	0

 

Máquinas de Estados

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;
entity Maq_Estados is
    Port ( clk,reset : in  STD_LOGIC;
          W : in  STD_LOGIC;
          Z : out  STD_LOGIC);
end Maq_Estados;
architecture Behavioral of Maq_Estados is
    type STATE_TYPE is (A, B, C);
    signal estado: STATE_TYPE;
```

```
begin
process(clk, reset)
begin
    if reset = '1' then
        estado <= A;
    elsif clk'event and clk = '1' then
        --Máquina de estados
        case estado is
            when A =>
                Z <= '0';
                if W = '1' then
                    estado <= B;
                end if;
            when B =>
                Z <= '0';
                if W = '0' then
                    estado <= A;
                else
                    estado <=C;
                end if;
            when C =>
                Z <= '1';
                if W = '0' then
                    estado <= A;
                end if;
            end case;
        end if;
    end process;
end Behavioral;
```

Máquinas de Estados: Testbench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY TB_ME IS
END TB_ME;
ARCHITECTURE behavior OF TB_ME IS
  -- Component Declaration for the Unit Under Test (UUT)
  COMPONENT Maq_Estados
  PORT (
    clk : IN std_logic;
    reset : IN std_logic;
    W : IN std_logic;
    Z : OUT std_logic
  );
  END COMPONENT;
  --Inputs
  signal clk : std_logic := '0';
  signal reset : std_logic := '0';
  signal W : std_logic := '0';
  --Outputs
  signal Z : std_logic;
  -- Clock period definitions
  constant clk_period : time := 10 ns;
BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: Maq_Estados PORT MAP (
    clk => clk,
    reset => reset,
    W => W,
    Z => Z
  );
```


```
  -- Clock process definitions
  clk_process :process
  begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
  end process;

  -- Stimulus process
  stim_proc: process
  begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    wait for clk_period*10;

    -- insert stimulus here

    wait;
  end process;
END;
```

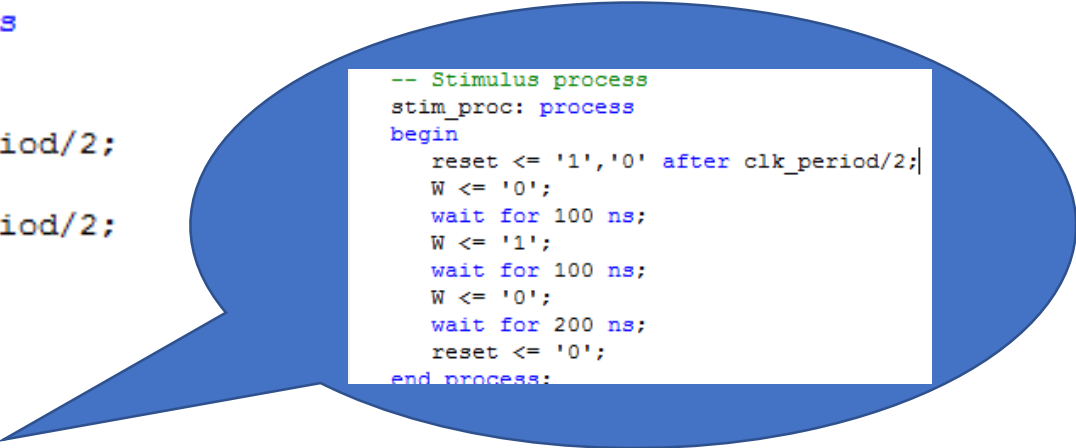

```
-- Stimulus process
stim_proc: process
begin
  reset <= '1','0' after clk_period/2;
  W <= '0';
  wait for 100 ns;
  W <= '1';
  wait for 100 ns;
  W <= '0';
  wait for 200 ns;
  reset <= '0';
end process;
```

Máquinas de Estados

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;
entity ME_Cont is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        Control : in  STD_LOGIC_VECTOR (1 downto 0);
        SaidaLeds : out  STD_LOGIC_VECTOR (3 downto 0);
        Display7 : out  STD_LOGIC_VECTOR (6 downto 0);
        c : out  STD_LOGIC);
end ME_Cont;

architecture Behavioral of ME_Cont is
  COMPONENT Mod_Display
  PORT( clk      : IN  STD_LOGIC;
        hex1     : IN  STD_LOGIC_VECTOR (3 DOWNTO 0);
        hex2     : IN  STD_LOGIC_VECTOR (3 DOWNTO 0);
        c        : OUT  STD_LOGIC;
        hex_out  : OUT  STD_LOGIC_VECTOR (6 DOWNTO 0);
        Reset    : IN  STD_LOGIC);
  END COMPONENT;

  type STATE_TYPE is (E0,E1, E2,E3);
  signal estado: STATE_TYPE := E0;
  signal hex_aux : STD_LOGIC_VECTOR (3 DOWNTO 0):="0000";
  signal q : STD_LOGIC_VECTOR (3 DOWNTO 0);
  signal up: STD_LOGIC :='0';
  signal tick: STD_LOGIC :='0';
  signal clk_aux: STD_LOGIC :='0';
begin
  timer: entity work.mod_m_counter(arch)
  GENERIC MAP(
    N =>26,M =>50000000)
  PORT MAP(
    clk => clk,
    reset => reset,
    max_tick => tick
  );
  Display: Mod_Display PORT MAP(
    clk => clk,
    hex1 => "1110",
    hex2 => hex_aux,
    c => c,
    hex_out => Display7,
    Reset => reset
  );

  counter: entity work.counter_up_down(arch)
  GENERIC MAP(N =>4)
  PORT MAP(
    clk => clk_aux,
    reset => reset,
    up => up,
    q => q
  );
  ME: process(clk, reset)
  begin
    if reset = '1' then
      estado <= E0;
      hex_aux <= "0000";
    elsif clk'event and clk = '1' then
      --Máquina de estados
      case estado is
        when E0 =>
          hex_aux <= "0000";
          if Control = "00" then
            estado <= E0;
            SaidaLeds<= "1010";
          else
            estado <= E1;
          end if;
        when E1 =>
          hex_aux <= "0001";
          if Control = "01" then
            estado <= E1;
            SaidaLeds<= "0101";
          else
            estado <= E2;
          end if;
        when E2 =>
          hex_aux <= "0010";
          if Control = "10" then
            estado <= E2;
            up <='0';
            SaidaLeds<= q;
          else
            estado <= E3;
          end if;
        when E3 =>
          hex_aux <= "0011";
          if Control = "11" then
            estado <= E3;
            up <='1';
            SaidaLeds<= q;
          else
            estado <= E0;
          end if;
      end case;
    end if;
  end process;

  tempo: process (tick)
  begin
    if (tick'event and tick='1') then
      clk_aux <= not clk_aux;
    end if;
  end process;
end Behavioral;
```